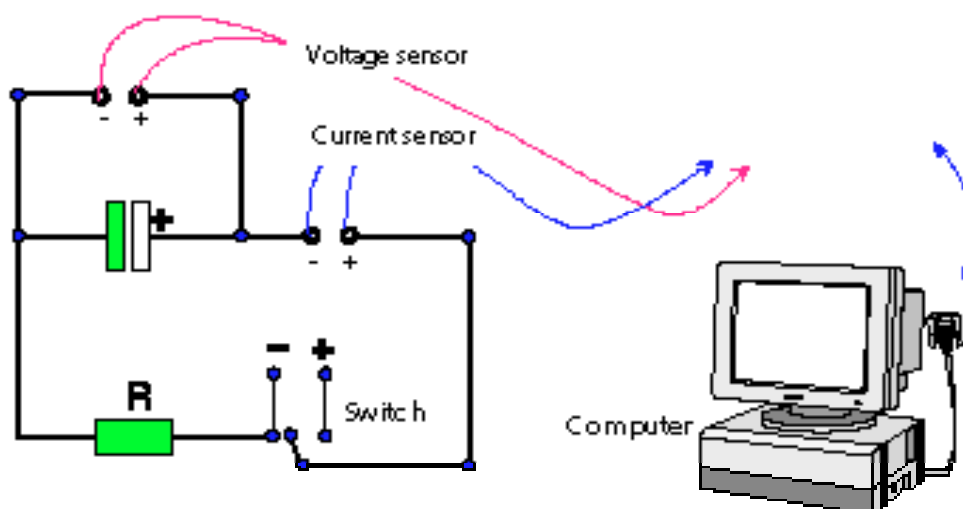


# Capacitor charge and discharge



The voltage & current of a capacitor are measured as it charges and discharges. Sensors allow a graph to be plotted as this happens. The effect of different values of the capacitor and resistor can easily be explored.

## Apparatus

1000 mF capacitor, 1k $\Omega$  resistor, power supply, switch, leads, voltage and current sensors, interface. You may need to 'bias' the voltage to get your readings on screen.

## Setting up

Connect the current sensor to socket 1, and the voltage sensor to socket 2.

If the sensors are adjustable set a 100mA range on the current sensor and a 10V range on the voltage sensor. Some systems recognise the sensors you attach automatically, in others you do this yourself.

## Recording the data

Record for 1 minute. Charge the capacitor and when charged, move the switch to allow it to discharge.

## Using the results

Describe the graph you see.

What does the graph tell you about the way a capacitor discharges?

What factors affect this?

Save your data on disc and print the graph.

